



HW4 REPORT



Ömer Faruk Bitikçioğlu - 161044010



I have already implemented ALU in the previous homework. In this homework I implemented the other components. Main control, ALU control and sign extend works correctly. But I am not sure about the register and data parts. When I connect all the components it didn't read instructions and compute anything. Unfortunately, I didn't have time to fix this issue.

I add the designs and calculations below. Also, you can check all my Verilog codes by using the .qar file.

Main Control

 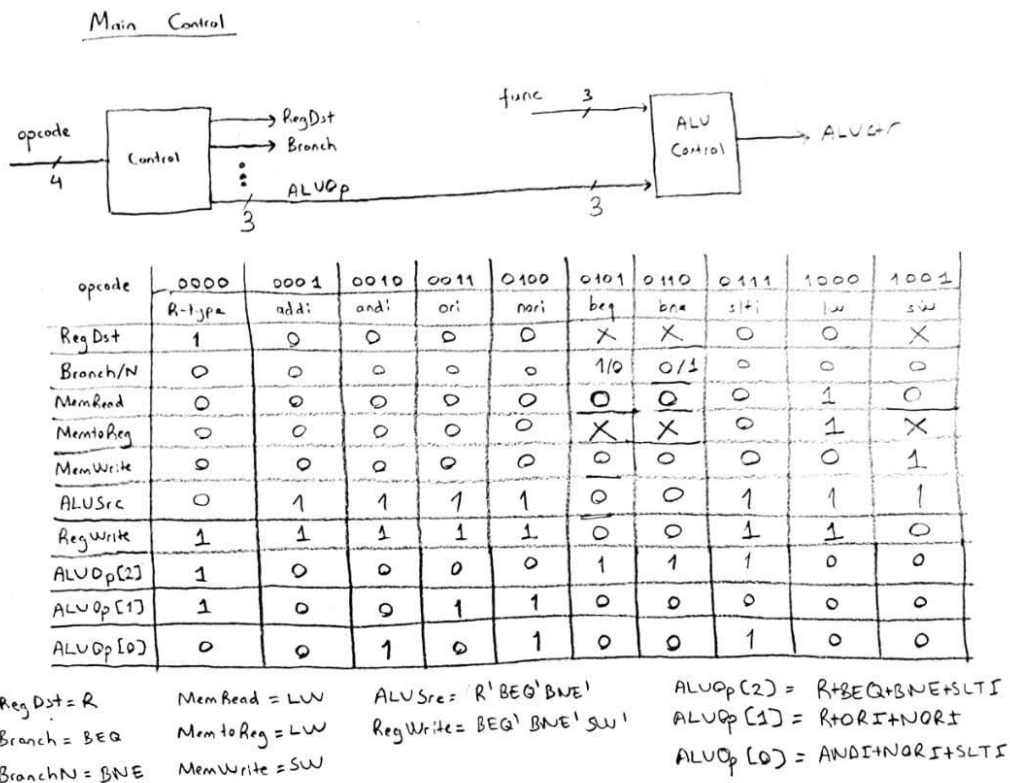


Control Unit Testbench

```
# time = 0, opcode= 0000, RegDst=1, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=0, RegWrite=1, ALUOp= 110
# time = 20, opcode= 0001, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 000
# time = 40, opcode= 0010, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 001
# time = 60, opcode= 0011, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 010
# time = 80, opcode= 0100, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 011
# time = 100, opcode= 0101, RegDst=0, Branch=1, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=0, RegWrite=0, ALUOp= 100
# time = 120, opcode= 0110, RegDst=0, Branch=0, BranchN=1, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=0, RegWrite=0, ALUOp= 100
# time = 140, opcode= 0111, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 101
# time = 160, opcode= 1000, RegDst=0, Branch=0, BranchN=0, MemRead=1, MemtoReg=1, MemWrite=0, ALUSrc=1, RegWrite=1, ALUOp= 000
# time = 180, opcode= 1001, RegDst=0, Branch=0, BranchN=0, MemRead=0, MemtoReg=0, MemWrite=1, ALUSrc=1, RegWrite=0, ALUOp= 000
```

ALU Control

Instruction	opcode	P2F1F0 ALUOp	F2F1F0 Function	Desired ALU action	C2 C1 C0 ALU control	
AND	0000	X 110	000	and	110 -	✓
ADD	0000	110	001	add	000	✓
SUB	0000	\ 110	010	sub	010 -	✓
XOR	0000	0 110	011	xor	001	✓
NOR	0000	0 110	100	nor	101	✓
OR	0000	0 110	101	or	111 -	✓
ADDI	0001	000	xxx	add	000	✓
ANDI	0010	\ 001	xxx	and	110 -	✓
ORI	0011	0 010	xxx	or	111 -	✓
NORI	0100	0 011	xxx	nor	101	✓
BEQ	0101	1 100	xxx	sub	010 -	✓
BNE	0110	1 100	xxx	sub	010 -	✓
SLTI	0111	1 101	xxx	slt	000	✓
LW	1000	000	xxx	add	000	✓
SW	1001	000	xxx	add	000	✓

 $C2 = P2P1F1'(F2 + F0') + P1'F0 + P2'P1$ $C1 = P2P1(F2'F0' + F2F0) + P2'(P1 \oplus F0) + P2P1'P0'$
 $C0 = P2P1(F2F1' + F1F0) + P2'P1$



ALU control testbench

```
# time = 0, ALUOp= 110, func= 000, ALUctr= 110
# time = 20, ALUOp= 110, func= 001, ALUctr= 000
# time = 40, ALUOp= 110, func= 010, ALUctr= 010
# time = 60, ALUOp= 110, func= 011, ALUctr= 001
# time = 80, ALUOp= 110, func= 100, ALUctr= 101
# time = 100, ALUOp= 110, func= 101, ALUctr= 111
# time = 120, ALUOp= 000, func= 000, ALUctr= 000
# time = 140, ALUOp= 001, func= 000, ALUctr= 110
# time = 160, ALUOp= 010, func= 000, ALUctr= 111
# time = 180, ALUOp= 011, func= 000, ALUctr= 101
# time = 200, ALUOp= 100, func= 000, ALUctr= 010
# time = 240, ALUOp= 101, func= 000, ALUctr= 100
# time = 260, ALUOp= 000, func= 000, ALUctr= 000
```

Sign Extend Testbench

```
# time = 0, imm= 001011, extended= 00000000000000000000000000001011
# time = 20, imm= 101010, extended= 11111111111111111111111111101010
```

Testbench of the broken processor:

```

# Instruction: xxxxxxxxxxxxxxxxx,
# RS Content:                xxx, RT Content:                xxx, RD Content:                xxx
# ---CONTROL SIGNALS---
# RegDst: x, Branch: x, BranchN: x, MemRead: x, MemtoReg: x, ALUOp: xxx, MemWrite: x, ALUSrc: x, RegWrite: x,
# PC :   x, clock :1
# Instruction: xxxxxxxxxxxxxxxxx,
# RS Content:                xxx, RT Content:                xxx, RD Content:                xxx
# ---CONTROL SIGNALS---
# RegDst: x, Branch: x, BranchN: x, MemRead: x, MemtoReg: x, ALUOp: xxx, MemWrite: x, ALUSrc: x, RegWrite: x,
# PC :   x, clock :0
# Instruction: xxxxxxxxxxxxxxxxx,
# RS Content:                xxx, RT Content:                xxx, RD Content:                xxx
# ---CONTROL SIGNALS---
# RegDst: x, Branch: x, BranchN: x, MemRead: x, MemtoReg: x, ALUOp: xxx, MemWrite: x, ALUSrc: x, RegWrite: x,
# PC :   x, clock :1

```