



COMPUTER ORGANIZATION

HOMEWORK 3




ÖMER FARUK BİTİKÇİOĞLU
161044010


Firstly, I found formulas for adder. Then I sketched alu32 on paper. Then I started to implement all the components to combine with alu32. To choose a value I implemented an 8x1 multiplexer.

adder			sum	cout
a	b	cin	sum	cout
1	1	1	1	1
1	1	0	0	1
1	0	1	0	1
1	0	0	1	0
0	1	1	0	1
0	1	0	1	0
0	0	1	1	0
0	0	0	0	0

$$\begin{aligned} \text{sum} &= abc_{in} + ab'c_{in}' + a'b c_{in}' + a'b'c_{in} \\ &= c_{in} (ab + a'b') + c_{in}' (ab' + a'b) \\ &= c_{in} (a \oplus b)' + c_{in}' (a \oplus b) \\ &= c_{in} \oplus (a \oplus b) \end{aligned}$$
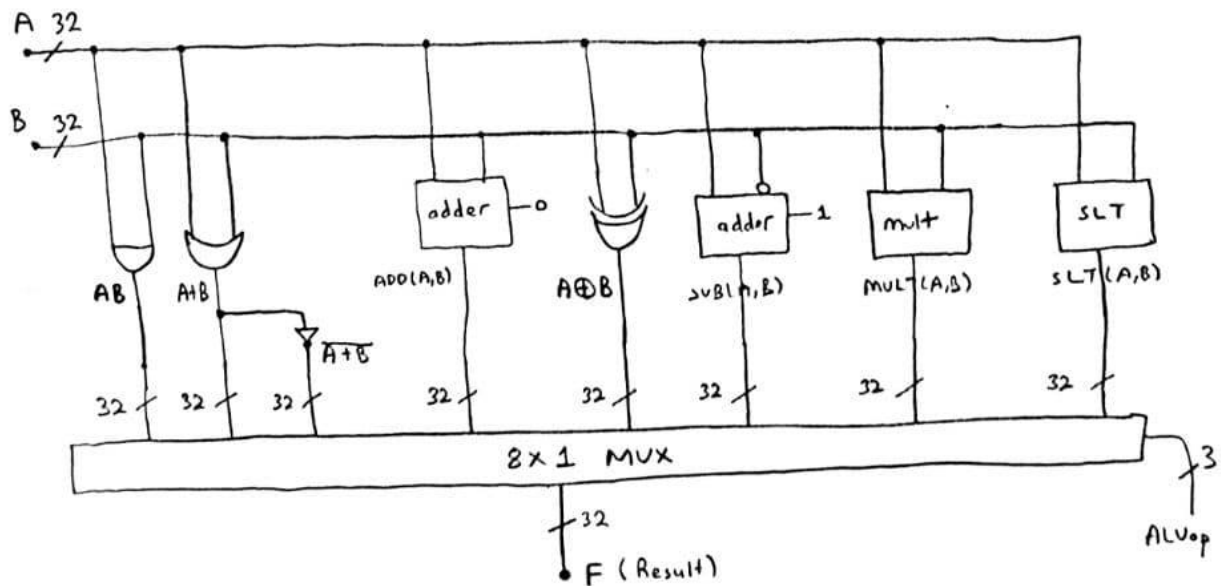
$$\begin{aligned} \text{cout} &= abc_{in} + abc_{in}' + ab'c_{in} + a'b c_{in} \\ &= ab(c_{in} + c_{in}') + c_{in} (ab' + a'b) \\ &= ab + c_{in} (a \oplus b) \end{aligned}$$


S ₂	S ₁	S ₀	Op	
0	0	0	ADD	X + S ₂ ' S ₁ ' S ₀ ' D ₀
0	0	1	XOR	X + S ₂ ' S ₁ ' S ₀ D ₁
0	1	0	SUB	X + S ₂ ' S ₁ S ₀ ' D ₂
0	1	1	MULT	X + S ₂ ' S ₁ S ₀ D ₃
1	0	0	SLT	X + S ₂ S ₁ ' S ₀ ' D ₄
1	0	1	NOR	X + S ₂ S ₁ ' S ₀ D ₅
1	1	0	AND	X + S ₂ S ₁ S ₀ ' D ₆
1	1	1	OR	X + S ₂ S ₁ S ₀ D ₇

 

Adder / full adder

To implement 32-bit adder, I used full adder and call it in a loop. To use carry in and find the exact carry out I separated the adding first and last bits.

Full adder testbench results:

```
# time = 0, a =0, b=0, carry_in=0, sum=0, carry_out=0
# time = 20, a =0, b=0, carry_in=1, sum=1, carry_out=0
# time = 40, a =0, b=1, carry_in=0, sum=1, carry_out=0
# time = 60, a =0, b=1, carry_in=1, sum=0, carry_out=1
# time = 80, a =1, b=0, carry_in=0, sum=1, carry_out=0
# time = 100, a =1, b=0, carry_in=1, sum=0, carry_out=1
# time = 120, a =1, b=1, carry_in=0, sum=0, carry_out=1
# time = 140, a =1, b=1, carry_in=1, sum=1, carry_out=1
```

Adder testbench results:

```
# time = 0, a =1111010001111110100010000001000, b=10110001110100101000110100001000, carry_in=0, sum=10100110010100011101000100010000, carry_out=1
# time = 20, a =1111010001111110100010000001000, b=10110001110100101000110100001000, carry_in=1, sum=10100110010100011101000100010001, carry_out=1
# time = 40, a =000111011000010010000000000010110, b=010101001010111000010100001000111, carry_in=0, sum=01110010001100101010100001011101, carry_out=0
# time = 60, a =000111011000010010000000000010110, b=010101001010111000010100001000111, carry_in=1, sum=01110010001100101010100001011110, carry_out=0
# time = 80, a =100010101111000011011101011001, b=0011000101100000100010111011010, carry_in=0, sum=10111100101010010011010100110011, carry_out=0
# time = 100, a =100010101111000011011101011001, b=0011000101100000100010111011010, carry_in=1, sum=10111100101010010011010100110100, carry_out=0
# time = 120, a =11111111000110001110010111100, b=10111110000011000101001100010100, carry_in=0, sum=10111101100110001100110010010000, carry_out=1
# time = 140, a =11111111000110001110010111100, b=10111110000011000101001100010100, carry_in=1, sum=10111101100110001100110010010001, carry_out=1
# time = 160, a =11000000001100010101101111001, b=0111100001000101110110011010011, carry_in=0, sum=0011100001101111001101011001100, carry_out=1
# time = 180, a =11000000001100010101101111001, b=0111100001000101110110011010011, carry_in=1, sum=0011100001101111001101011001101, carry_out=1
# time = 200, a =100110101111001101100011011101, b=0011101010100111101001010001110, carry_in=0, sum=11010101101000011000010001101011, carry_out=0
# time = 220, a =100110101111001101100011011101, b=0011101010100111101001010001110, carry_in=1, sum=11010101101000011000010001101100, carry_out=0
# time = 240, a =110111111010110101010101000010101, b=10100010001100110101000101001010, carry_in=0, sum=100000100000100111110110101111, carry_out=1
# time = 260, a =110111111010110101010101000010101, b=10100010001100110101000101001010, carry_in=1, sum=1000001000001001111101101100000, carry_out=1
# time = 280, a =01010000111100100001101010110110, b=0011011111101001011101001010100, carry_in=0, sum=10001000111001101101010100001010, carry_out=0
# time = 300, a =01010000111100100001101010110110, b=0011011111101001011101001010100, carry_in=1, sum=10001000111001101101010100001011, carry_out=0
```

Or32 / Xor32 / And32

I used dynamic programming to solve these. I downgraded the problem to 16-bit, 8-bit and 4-bit then combine the results.

And32 testbench results:

```
# time = 0, in1= 1111010001111110100010000001000, in2= 10110001110100101000110100001000, and= 10110000010100100000010000001000
# time = 40, in1= 000111011000010010000000000010110, in2= 01010100101011100010100001000111, and= 00010100100001000000000000000110
# time = 60, in1= 100010101111000011011101011001, in2= 0011000101100001100010111011010, and= 000000001011000001000010101011000
# time = 80, in1= 111111110001100011100101111100, in2= 10111110000011000101001100010100, and= 10111110000011000101000100010100
# time = 100, in1= 1100000000110001101011011111001, in2= 0111100001000101110110011010011, and= 0100000000000001010110011010001
```

Or32 testbench results:

```
# time = 0, in1= 1111010001111110100010000001000, in2= 10110001110100101000110100001000, or= 11110101111111100110100001000
# time = 40, in1= 000111011000010010000000000010110, in2= 01010100101011100010100001000111, or= 01011101101011101010100001010111
# time = 60, in1= 100010101111000011011101011001, in2= 0011000101100001100010111011010, or= 1011011111100001100111011011011
# time = 80, in1= 111111110001100011100101111100, in2= 10111110000011000101001100010100, or= 111111110001100011101101111100
# time = 100, in1= 1100000000110001101011011111001, in2= 0111100001000101110110011010011, or= 11111000011010111011011111011
```

Xor32 testbench results:

```
# time = 0, in1= 1111010001111110100010000001000, in2= 10110001110100101000110100001000, xor= 010001011010111011100100100000000
# time = 40, in1= 000111011000010010000000000010110, in2= 01010100101011100010100001000111, xor= 010010010010101010101000001010001
# time = 60, in1= 100010101111000011011101011001, in2= 0011000101100001100010111011010, xor= 10111011010010001010101010000011
# time = 80, in1= 111111110001100011100101111100, in2= 10111110000011000101001100010100, xor= 01000001100000000010101001101000
# time = 100, in1= 1100000000110001101011011111001, in2= 0111100001000101110110011010011, xor= 1011100001101000100000100101010
```

Sub32

To subtract B from A, I get the two's complement of B, then I added it to A. So, I didn't need to implement a new component. I used adder.

Sub32 testbench results:

```
# time = 0, A= 1111010001111110100010000001000, B= 10110001110100101000110100001000, sub= 01000010101011001011101100000000
# time = 40, A= 000111011000010010000000000010110, B= 01010100101011100010100001000111, sub= 1100100011010110010101111001111
# time = 60, A= 100010101111000011011101011001, B= 0011000101100001100010111011010, sub= 0101100101000111010100101111111
# time = 80, A= 111111110001100011100101111100, B= 10111110000011000101001100010100, sub= 0100000110000000000100110011000
# time = 100, A= 1100000000110001101011011111001, B= 0111100001000101110110011010011, sub= 0100011111101111000001001001101
```

Not32

Simply I used the not gate for 32 times in a loop.

Not32 testbench results:

```
# time = 0, inp= 11110100011111110100010000001000, not= 00001011100000001011101111110111
# time = 20, inp= 10110001110100101000110100001000, not= 01001110001011010111001011110111
# time = 40, inp= 11110100011111110100010000001000, not= 00001011100000001011101111110111
# time = 60, inp= 10110001110100101000110100001000, not= 01001110001011010111001011110111
# time = 80, inp= 0001101100001001000000000010110, not= 1110001001111011011111111101001
# time = 100, inp= 01010100101011100010100001000111, not= 10101011010100011101011110111000
# time = 120, inp= 1000101011110000110111101011001, not= 0110101000001111001000010100110
# time = 140, inp= 00110001101100001100010111011010, not= 11001110010011110011101000100101
# time = 160, inp= 1111111100011000111100101111100, not= 00000000011100111000011010000011
# time = 180, inp= 10111110000011000101001100010100, not= 01000001111100111010110011101011
# time = 200, inp= 1100000000110001101011011111001, not= 0011111110011100101001000000110
# time = 220, inp= 01111000010001011110110011010011, not= 10000111101110100001001100101100
```

Set on Less Than

I subtracted B from A, then checked for the most significant bit. If $A < B$, then the result of $A-B$ must be negative (most significant bit = 1).

SLT testbench results:

```
# time = 0, A= 11110100011111110100010000001000, B= 10110001110100101000110100001000, slt= 00000000000000000000000000000000
# time = 20, A= 1111101011110000110111101011001, B= 00000001101100001100010111011010, slt= 00000000000000000000000000000001
# time = 40, A= 0010001110110001001010101010001, B= 00100101101100101100010111011000, slt= 00000000000000000000000000000001
# time = 60, A= 1111111100011000111100101111100, B= 10111110000011000101001100010100, slt= 00000000000000000000000000000000
# time = 80, A= 1100000000110001101011011111001, B= 00001000010001011110110011010011, slt= 00000000000000000000000000000001
```

8x1 Multiplexer

This module selects the desired bit and sends it to F. The formula is on the bottom of the paper that I put on the first page of this report.

8x1mux testbench results:

```
# time = 0, D0= 1, D1= 0, D2= 0, D3= 0, D4= 0, D5= 1, D6= 1, D7= 1, S= 000, F= 1
# time = 20, D0= 0, D1= 1, D2= 1, D3= 0, D4= 1, D5= 1, D6= 1, D7= 1, S= 001, F= 1
# time = 40, D0= 1, D1= 0, D2= 1, D3= 0, D4= 0, D5= 0, D6= 0, D7= 1, S= 010, F= 1
# time = 60, D0= 0, D1= 1, D2= 0, D3= 1, D4= 1, D5= 1, D6= 1, D7= 0, S= 011, F= 1
# time = 80, D0= 0, D1= 1, D2= 1, D3= 1, D4= 1, D5= 1, D6= 0, D7= 1, S= 100, F= 1
# time = 100, D0= 1, D1= 0, D2= 0, D3= 0, D4= 1, D5= 0, D6= 1, D7= 1, S= 101, F= 0
# time = 120, D0= 0, D1= 0, D2= 1, D3= 1, D4= 0, D5= 0, D6= 0, D7= 0, S= 110, F= 0
# time = 140, D0= 0, D1= 1, D2= 0, D3= 0, D4= 1, D5= 1, D6= 0, D7= 0, S= 111, F= 0
```

ALU32

I combined all the modules and selected the desired results with multiplexer.

Alu32 testbench results:

```
# time = 0, A= 11110100011111110100010000001000, B= 10110001110100101000110100001000, ALUop= 000, F= 10100110010100011101000100010000
# time = 20, A= 1111101011110000110111101011001, B= 00000001101100001100010111011010, ALUop= 001, F= 11111011010010001010101010000011
# time = 40, A= 0010001110110001001010101010001, B= 00100101101100101100010111011000, ALUop= 010, F= 111111011111110011001101111001
# time = 60, A= 1111111100011000111100101111100, B= 10111110000011000101001100010100, ALUop= 011, F= xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx
# time = 80, A= 1100000000110001101011011111001, B= 00001000010001011110110011010011, ALUop= 100, F= 00000000000000000000000000000001
# time = 100, A= 0011111101011101101101010011011, B= 1000010010011101111011110110011, ALUop= 101, F= 0100000001000000000000001000100
# time = 120, A= 1011000111100011011010000101111, B= 1101101000000010110000001001111, ALUop= 110, F= 1001000000000010010000000001111
# time = 140, A= 0010001100010000000001111110011, B= 10001011110101000101001101000110, ALUop= 111, F= 1010101111010100010101111110111
```

Last words

- All the implemented modules work fine.
- Nor is simply not of or.
- If you are getting wrong results, it probably because of overflowing 32-bits.
- Multiplier is not implemented.