

# Homework 3

CSE 232

May 2021

Draw a state diagram for an FSM with an input  $a$  and three outputs,  $x$ ,  $y$  and  $z$ . The  $xyz$  outputs generate a sequence in order 000, 011, 111, 010, 001, 101, 100, repeat. The output should change only on a rising clock edge when the input  $a = 1$ . Make the initial state 000.

Design your solution in five steps

Step 1: Create FSM

Step 2: Obtain architecture

Step 3: Encode states

Step 4: Generate state table

Step 5: Obtain Boolean expressions and draw controller

(Hint, at Step 5, you may use K-maps for simplifications)