

Homework 4

CSE 232

May 2021


1-) Define MUX size

There are 4 operations: Load, swap, clear, and maintain current state. So, we should use 4×1 MUX.

2-) Create MUX table

S_1	S_0	Operation
0	0	Maintain current state
0	1	Swap
1	0	Load
1	1	Clear

3-) Connect MUX Input

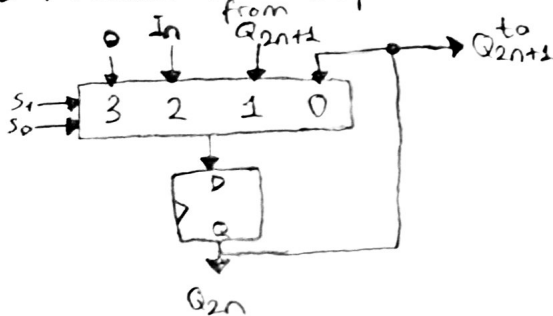



4-) Map control Lines

$cl > ld > sw$ (priorities)

Inputs			Outputs		Operation
cl	ld	sw	S_1	S_0	
0	0	0	0	0	Maintain current state
0	0	1	0	1	Swap
0	1	X	1	0	Load
1	X	X	1	1	Clear

$$S_1 = cl'ld + cl$$

$$S_0 = cl'ld'sw + cl$$

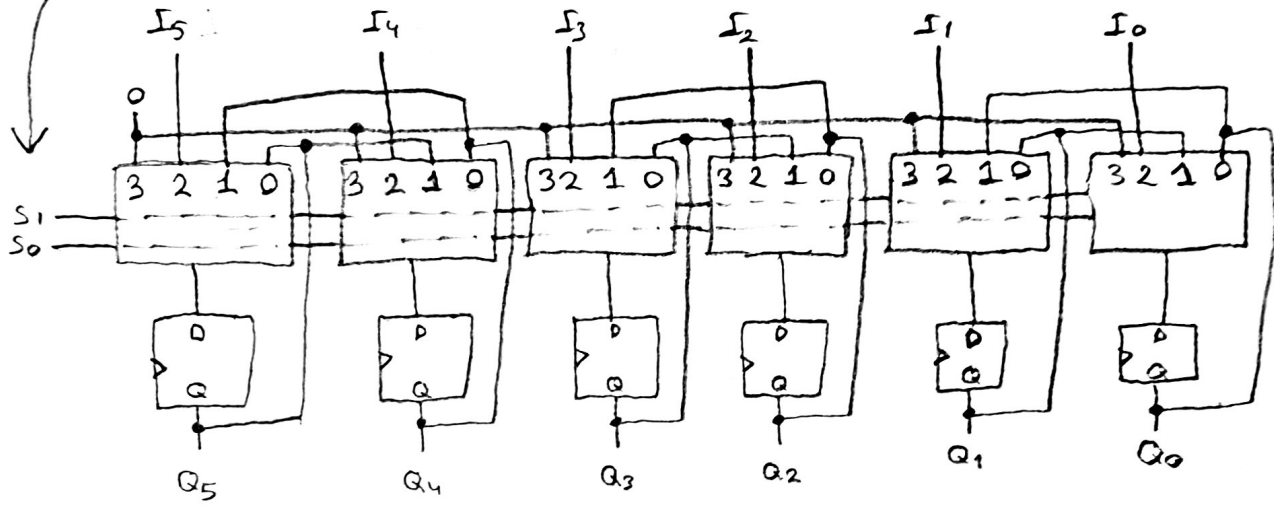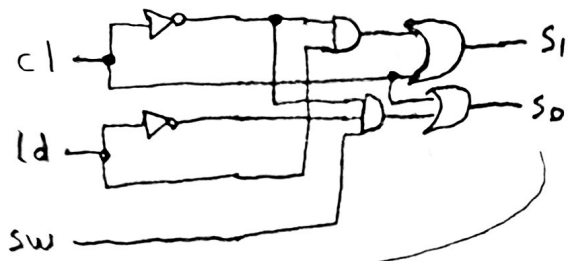

Ömer Faruk Bitikçioglu
161044010